

**1) Wiring techniques:**

One technique to help you avoid wiring errors is to make a photocopy of your design. Then, as you connect wire after wire, use an accent marker to color in each completed connection. Another thing you can do is to place a piece of tape or a small peel-off label indicating the unit number on each chip. Now, checking the connection U2-3 to U3-9 (or just 2-3 to 3-9) becomes quick and easy. Take your time making these connections. Most of the problems encountered in lab are not due to bad chips (although many people tend to blame their trouble on the chips).

By far the most common causes of trouble are incorrect or missing connections. And one of the things that make it so difficult to spot a bad connection is the "spaghetti" or "ramen" approach to wiring: dozens of wires arching over the chips like a dense mass of cold, stiff noodles. This makes it hard to see where the wires go, and nearly impossible to remove a chip if one should turn out to be bad after all.

The alternative to spaghetti wiring is to cut all wires to the proper length, run them flat along the board with each bend at 90 degrees (you will have to leave room between the chips for the wires). Of course, this takes time to do and nobody wants to bother. But the savings in time and effort later when you are troubleshooting will make it all seem worthwhile. Your breadboard should come with a wire kit containing pre-cut wires with stripped and bent ends. Each of these spans an integral number of holes. Instead of bending a long wire around a corner, just insert two shorter lengths of wire at right angles to each other. Insertion and removal is done quickly and easily with a pair of tweezers or needle-nose pliers.

-----

**2) Debugging Combinational Circuits:**

A combinational circuit is one with no flip-flops or latches. You usually become aware of problems in combinational circuits when a check reveals that one or more outputs are at the wrong logic levels. The problem may be some or all of the following:

- the circuit contains one or more bad elements.
- you forgot to make certain connections.
- you made some incorrect connections.

The search for the source of trouble begins with finding an input combination that produces an incorrect output. For this input combination, check your wiring diagram and determine what the correct values should be at the inputs and outputs of each gate involved in producing the output value. With a logic probe, begin working backwards from the output, checking the value on each pin and using your wiring diagram "pinout" to guide you from pin to pin.

Example: you are checking a NAND gate whose output should be high. Instead you find that it is low. Check the inputs. Usually, if a NAND output is low, all inputs should be high; but, if at least one input is low, the gate may be bad. Otherwise, if they are all high, the gate is probably ok but at least one of the circuits that produce the gate inputs is not. Check these circuits the same way.

Occasionally your logic probe fails to indicate either high or low. Possible explanations are:

- Bent Pin:** if you get no indication when the probe touches a chip pin, the pin may be bent up under the chip and not in its hole (or the pin may be broken off).
- Input Pin Connected to Only Inputs:** check to see if a connecting wire which is supposed to go to an output pin actually goes to another input by mistake. If connections are made only to inputs, there will be no voltage to light up the probe.
- Output Pin Connected to Another Output:** if one output is high and the other low, the resulting voltage may be in-between (neither logic-1 nor logic-0), so a logic probe will indicate nothing. To check for this, disconnect all wires from the output of interest. If the probe now lights up, see if any of the wires went to another output by mistake.

### 3) Debugging Sequential Circuits:

A sequential circuit (made up of flip-flops, like a counter) is designed to go through a particular sequence of states. Suppose at some point it makes an incorrect state transition. The wrong way to start debugging this circuit would be to begin an exhaustive check of all connections and voltage levels. There is a more efficient, logical approach. For the sake of example, consider a 4-bit synchronous sequential circuit with D-flip-flops WXYZ. Each time the circuit is clocked, inputs,  $D_w, D_x, D_y, D_z$  are loaded into the flip-flops. Thus the next-state values of flip-flop outputs WXYZ are the same as the present-state values of their inputs.

Assume flip-flops WXYZ are designed to follow the sequence  $\dots 0010 \rightarrow 0100 \rightarrow 1010 \dots$ . Now, suppose from state 0100, the circuit's next state goes to 1000, instead of 1010 as desired. In other words:

Desired sequence					Actual sequence			
W	X	Y	Z		W	X	Y	Z
0	0	1	0	↓	0	0	1	0
0	1	0	0	↓	0	1	0	0
1	0	1	0	↓	1	0	0	0

To locate the problem in a logical and systematic way, try the following approach:

- First go back to your design. Verify that your state table is correct. Do the same for the maps and for the algebraic expressions derived from the maps. Checking your design on paper is usually much simpler than debugging the hardware.
- If the design seems ok, place your circuit in the state from which the incorrect transition is made. In the example we are using, this would be state  $WXYZ = 0100$ . Notice that in going from 0100 to 1000, all flip-flops undergo the designed-for transition except Y, which fails to go high. Therefore, the obvious place to check is input  $D_y$  (while still in state 0100).

- c) When you check with the 'scope or logic probe, you expect to find  $D_y$  low since  $Y$  stays low after the next clock pulse. If, instead, you find  $D_y$  to be high, there may be something wrong with the flip-flop. But, if it *is* low, go back and make sure you didn't design  $D_y$  to be low by mistake.
- d) Now, if your design is ok, the problem must lie with the circuit that produces  $D_y$ . If  $D_y$  comes from the output of a gate, go back to Section 3 (Debugging Combinational Circuits), above. Start by checking the wire that connects  $D_y$  to the gate. If the wire is properly connected, then check the gate and its inputs, etc..
- e) When working with sequential circuits, make sure that your asynchronous preset and clear inputs are connected to the supply voltage (5V) if they are not being used.

---

A final word: efficient debugging requires practice as well as theoretical knowledge. You already have the theory, and you'll be surprised at how your self-confidence grows with a bit of practice and a few small successes. So when your circuit doesn't work as planned, don't throw up your hands. Pick up your logic probe and find the bug.